

Name: _____ Date: _____

Calculating Total Resistance ①

Calculate the total resistance (R_T) for the following combinations of resistors.

