

Name: \_\_\_\_\_

Date: \_\_\_\_\_

### Calculating Total Resistance <sup>(3)</sup>

Calculate the total resistance ( $R_T$ ) for the following combinations of resistors.

